

Lab 8: Flip-flops and Counter

Objective: To implement a RS latch and a binary counter with D-type flip flops.

Provided: 74X374 (D flip-flops), 7400 (quad 2-input NAND), 7404 (NOT), 7408 (AND), 7432 (OR), breadboard.

8.1 Experiment: RS Latch

Build an SR latch using 2 NAND gates (Figure 5-4(a), page 250, 6th Edition of Mano and Ciletti book). Demonstrate your circuit to the instructor. Do your observations agree with what you expect (Figure 5-4(b))? Explain why the input S=0 R=0 should be forbidden.

8.2 Experiment: Binary Counter

Design a binary counter that counts from 0 to 5 then back to 0 and repeat, display the count on LEDs.

1. Examine the pin-out diagram of the 74X374.

74374

8-bit 3-state D flip-flop.

+---+---+---+				+---+---+---*---+			
/OE	1	+++	20 VCC	/OE CLK D	Q		
Q1	2		19 Q8	=====	=====	=====	=====
D1	3		18 D8	1 X X Z			
D2	4		17 D7	0 / 0 0			
Q2	5	74	16 Q7	0 / 1 1			
Q3	6	374	15 Q6	0 !/ X -			
D3	7		14 D6	+	+	+	+
D4	8		13 D5				
Q4	9		12 Q5				
GND	10		11 CLK				
+-----+							

2. Start by filling the following table:

$Q_3(t)$	$Q_2(t)$	$Q_1(t)$	D_3 $Q_3(t+1)$	D_2 $Q_2(t+1)$	D_1 $Q_1(t+1)$
0	0	0	0	0	1

- Next, draw Karnaugh maps to find boolean expressions for each D input in terms of $Q_3(t)$, $Q_2(t)$, and $Q_1(t)$. Mark the inputs from 110 and 111 as don't care conditions in the state table and K-maps.
- Connect the 4-bit output of the counter to the LEDs.